

TED (15) – 4032

(REVISION — 2015)

Reg. No.....

Signature

DE & MP. #3.

DIPLOMA EXAMINATION IN ENGINEERING/TECHNOLOGY/
MANAGEMENT/COMMERCIAL PRACTICE — OCTOBER, 2017

DIGITAL ELECTRONICS AND MICROPROCESSOR

[Time : 3 hours

(Maximum marks : 100)

PART — A

(Maximum marks : 10)

Marks

I Answer *all* questions in one or two sentences. Each question carries 2 marks.

1. Write the BCD equivalent of decimal number $(108.37)_{10}$
2. Draw the circuit symbol and write the truth table of a negative edge triggered D Flip Flop.
3. Construct the structure of a 2 variable Karnaugh Map and map the following expression in it.

$$Y = \bar{A}\bar{B} + \bar{A}B$$

4. With the help of diagrams show the difference between a synchronous counter and an asynchronous counter with reference to the application of CLOCK signal.
5. List any four general purpose registers of 8085. (5×2 = 10)

PART — B

(Maximum marks : 30)

II Answer any *five* of the following questions. Each question carries 6 marks.

1. Perform the following operation in binary
 $(1101.101)_2 + (111.011)_2$.
2. Convert the decimal number $(3289.32)_{10}$ to binary number. Show the steps.
3. Write the truth table of a Full Adder Circuit. Construct it using AND, OR, EX-OR gate combinations.
4. Construct a positive edge triggered clocked ACTIVE HIGH R-S flip-flop with NAND gates and write its truth table.

5. Explain MOD Number of a counter. Determine the number of flip-flops required to construct a MOD - 10 Counter.
6. Implement a MOD 8 Synchronous Binary UP counter and write its count sequence. (Use negative edge-triggered JK flip-flops).
7. Explain with examples any three addressing modes of 8085 Microprocessor. (5×6 = 30)

PART — C

(Maximum marks : 60)

(Answer one *full* question from each unit. Each full question carries 15 marks.)

UNIT — I

- III (a) Execute the following operations in Two's Complement Method. Convert the result back to decimal number. (Use 8 bit format)
- (i) $(95)_{10} - (68)_{10}$ (ii) $(68)_{10} - (95)_{10}$ 10
- (b) Compare the TTL, ECL and CMOS Logic families on the basis of Propagation Delay, power dissipation, fan in and fan-out capability. 5

OR

- IV (a) List the basic gates in digital circuits. With the aid of truth tables and symbols describe their operation. Write the expression for their output. 10
- (b) Execute the following operation in binary.
- (i) $(110101.11)_2 / (101)_2$ (ii) $(10.111)_2 \times (1010)_2$ 5

UNIT — II

- V (a) Draw the schematic symbol of a positive edge triggered JK Flip Flop and write its truth table. Implement it using NAND gates only. 10
- (b) Simplify the following boolean expression using K map.
- $$Y = \bar{A}\bar{B}C + \bar{A}BC + ABC + A\bar{B}C + A\bar{B}\bar{C}$$
- 5

OR

- VI (a) NAND & NOR gate are called universal gates. Justify your answer with the help of examples. 10
- (b) Apply De Morgan's Theorems to the following expression and simplify it. Implement the simplified circuit using basic gates.
- $$Y = \overline{(A + \bar{B})(C + \bar{D})}$$
- 5

UNIT — III

- VII Implement a DECADE Ripple UP counter with a negative edge-triggered *J-K* flip-flops and write its count sequence with the waveforms. 15

OR

- VIII (a) Draw a Serial in Parallel Out Right Shift Register and explain how a data 1011 is stored in a register (use positive edge triggered D Flip Flop). 10
 (b) Explain with diagram the concept of R-2R Ladder Network for Digital to Analogue conversion. 5

UNIT — IV

- IX (a) Construct the PIN OUT diagram of 8085 Microprocessor and label all the pins. 10
 (b) Explain the following pin functions with reference to 8085 Microprocessor.
 (i) IO/\bar{M} (ii) ALE 5

OR

- X (a) Explain the following with reference to 8085 Microprocessor.
 (i) Flag Register.
 (ii) Arithmetic & Logic Unit.
 (iii) Program Counter.
 (iv) Stack Pointer. 10
 (b) Describe with examples the following instructions in 8085.
 (i) ADD (ii) ADC 5
-