

TED (15) – 3031

Reg. No.....

(REVISION — 2015)

Signature .....

DIPLOMA EXAMINATION IN ENGINEERING/TECHNOLOGY/  
MANAGEMENT/COMMERCIAL PRACTICE — OCTOBER, 2019

**ANALOG DEVICES & CIRCUITS**

[Time : 3 hours]

(Maximum marks : 100)

PART — A

(Maximum marks : 10)

Marks

I Answer *all* questions in one or two sentences. Each question carries 2 marks.

1. Define the term peak inverse voltage.
2. Name three schemes of amplifier coupling.
3. State Barkhausen's criteria for oscillation.
4. Draw the circuit of an op-amp integrator.
5. Define CMRR.

(5×2 = 10)

PART — B

(Maximum marks : 30)

II Answer any *five* of the following questions. Each question carries 6 marks.

1. Explain a full wave bridge rectifier.
2. Explain a zener diode voltage regulator.
3. Explain a transformer coupled amplifier.
4. Explain class A, class B and class C amplifier.
5. Explain a RC phase shift oscillator circuit.
6. Explain the working of colpitts oscillator.
7. List the characteristics of an ideal op amp.

(5×6 = 30)



## PART — C

(Maximum marks : 60)

(Answer *one* full question from each unit. Each full question carries 15 marks.)

## UNIT — I

- III (a) Explain a center tapped full wave rectifier circuit with waveform. 8  
 (b) Explain a LC filter. 7

OR

- IV (a) Explain the working of voltage regulator using IC7805. 7  
 (b) Explain a positive clipper using series diode. 8

## UNIT — II

- V (a) Explain a RC coupled amplifier and plot the frequency response. 8  
 (b) Distinguish between different coupling schemes used in multistage amplifiers. 7

OR

- VI (a) Explain the working of a complementary symmetry pushpull amplifier. 8  
 (b) Compare voltage and power amplifier. 7

## UNIT — III

- VII (a) Explain an astable multivibrator using IC 555. 8  
 (b) Explain the working of crystal oscillator. 7

OR

- VIII (a) Name the three multivibrators and give applications of each. 7  
 (b) Explain the working of Hartley oscillator. 8

## UNIT — IV

- IX (a) Explain a inverting amplifier using op-amp. 7  
 (b) Explain a summing amplifier using op-amp. 8

OR

- X (a) Explain a comparator using op-amp. 8  
 (b) Explain a differentiator using op-amp. 7
-